

TITLE : conduct an experiment to understand the working principle of

Expt No. : 1

Date : 15/03/22

i) potentiometer

ii) comparator



components required:-

a.	Multimeter - 1
b.	Wire - 2
c.	Bread Board - 1
d.	Resistor - 2
e.	Trainer Kit - 1

Color Resistor	1st Band	2nd Band	3rd Band	Multiplier	Tolerance
Black	0	0	0	$\times 1$	—
Brown	1	1	1	$\times 10$	1%.
Red	2	2	2	$\times 100$	—
Orange	3	3	3	$\times 1000$	—
Yellow	4	4	4	$\times 10^4$	—
Green	5	5	5	$\times 10^5$	—
Blue	6	6	6	$\times 10^6$	—
Violet	7	7	7	—	—
Grey	8	8	8	—	—
White	9	9	9	—	—
Gold	—	—	—	—	—
Silver	—	—	—	—	5%.
None	—	—	—	—	10%.

Marks :

Staff :

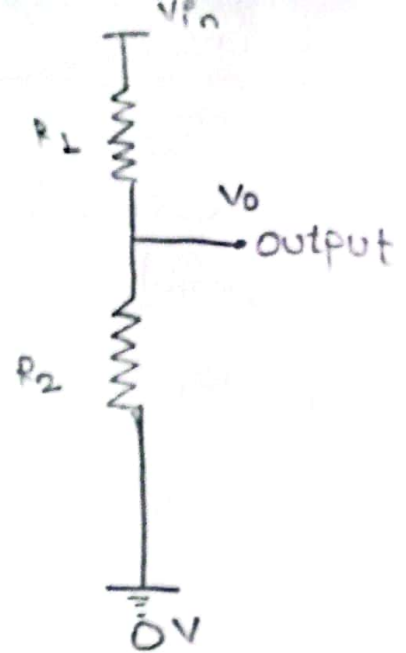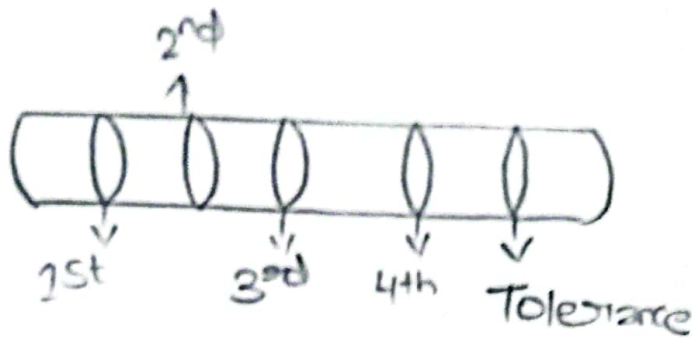

Tolerance = Variation in resistance

Problems:- i. $R_1 = 1k\Omega$
 $R_2 = 1k\Omega$
 $V_{in} = 5V$

$$V_o = \frac{5 \times 1}{1 + 1} = \frac{5}{2} = 2.5V$$

ii. $V_o = 1V$
 $V_{in} = 5V$
 $R_1 = 1k\Omega$
 $R_2 = ?$

$$V_o = \frac{5 \times R_2}{1 + R_2}$$

$$1 = \frac{5R_2}{1 + R_2}$$

$$1 + R_2 = 5R_2$$

$$R_2 = \frac{1}{4} = 0.25\Omega$$

iii) $V_{in} = 5V$, $R_1 = 1k\Omega$, $R_2 = 2k\Omega$ and $V_o = ?$

$$V_o = \frac{5 \times 2}{1 + 2} = \frac{10}{3} = 3.33\Omega$$

Result:- Understood the working principle of potentiometer and verified successfully.

TITLE : _____

Expt No. : 1

Date : 15/09/2022

$$V_0 = \frac{V_{in} \times R_2}{R_1 + R_2}$$

[R_2 = opposite Resistance]

$$R_1 = 1k2.4 \Omega$$

$$R_2 = 46.4 \Omega$$

$$V_0 = 4.81$$

$$V_{in} = 5V$$

Procedure i) collect the components necessary to complete the circuit.

ii) connect ~~to~~ two resistors i.e. R_1 and R_2 in series.

iii) Connect DC power supply 5V/~~or~~ 10V/12V to one point of resistor i.e. R_1 .


iv) Connect ground (Gnd) and other terminal of resistor i.e. R_2 .

v) After finishing the circuit take the reading or note down the readings from Multimeter.

vi) Repeat the above steps by taking the different resistors values.

Marks :



Staff :

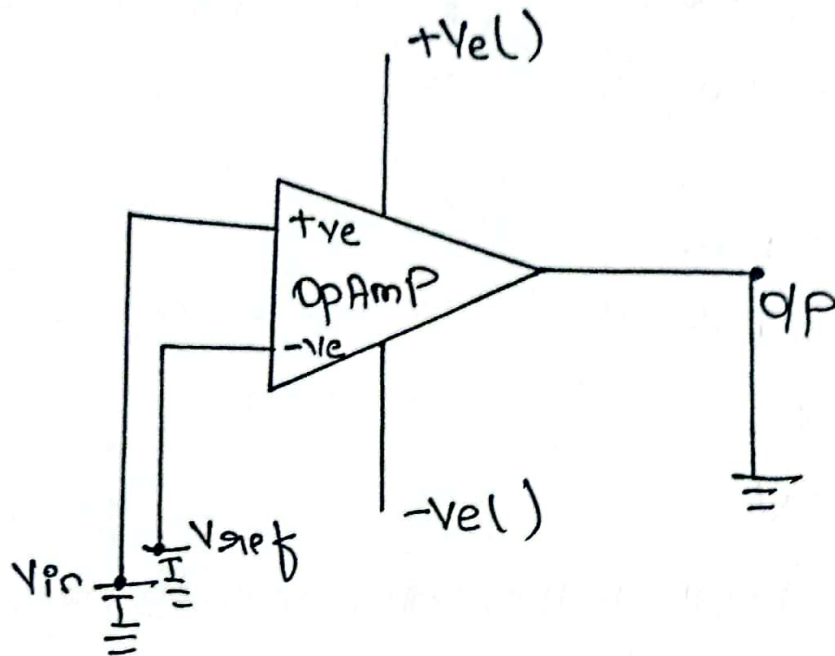

$V_{in} > V_{ref}$ the O/P = $+Ve$

$V_{in} < V_{ref}$ the O/P = $-Ve$

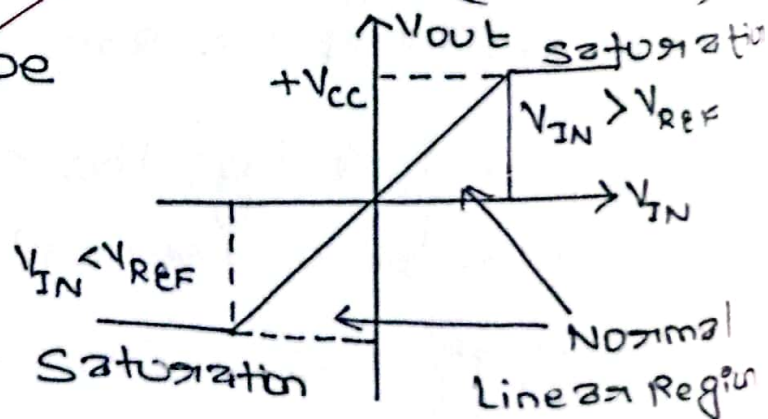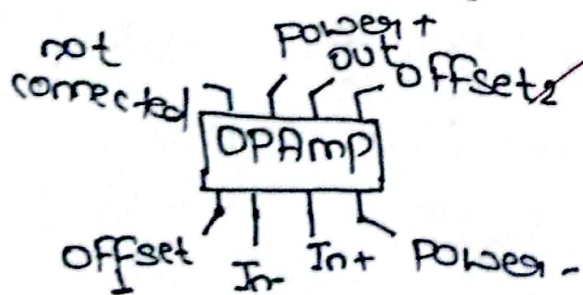- Input voltage is always should be less than ($+Ve$ or $-Ve$)
- CRO: Cathode Ray Oscilloscope



TITLE : b) Comparator

Expt No : 16

Date : 20/09/22

components Required:-

S. NO.	component	Quantity
1	IC741(OpAmp)	1
2	Power supply	34
3	Multimeter	1
4	connecting wires	-
5	Bread Board	1

Procedure:- i) First of all, collect all the components necessary to complete the circuit.

ii) Connect IC741(OpAmp) in Bread Board horizontally.

iii) Ic has 8 pins but 4 pin is not connected; connect 4 power supply in respect pins.

iv) 1st power supply in In-; 2nd, 3rd and 4th in In+, power- and power+ with positive wire

v) Connect all the negative wires in ground (gnd)

vi) Now, connect Multimeter in output (positive one) and connect negative to Ground (Gnd).

Marks :

Staff :

TITLE Liquid sensor

Expt No 2

Date 23/09/22

AIM:-

- conduct an experiment to determine the sensitivity of the liquid sensor.
- Design a system to indicate the petrol level in the vehicle using liquid level sensor.

~~Circuit Diagram:-~~




Components Required:-

S.No	Components Name	Quantity
1	Water level sensor	1
2	Bread Board	1
3	Buzzer	1
4	LED	1
5	Connecting wires	2
6	Trainer Kit	1
7	Multimeter	1

Marks :

Staff :

Circuit Diagram

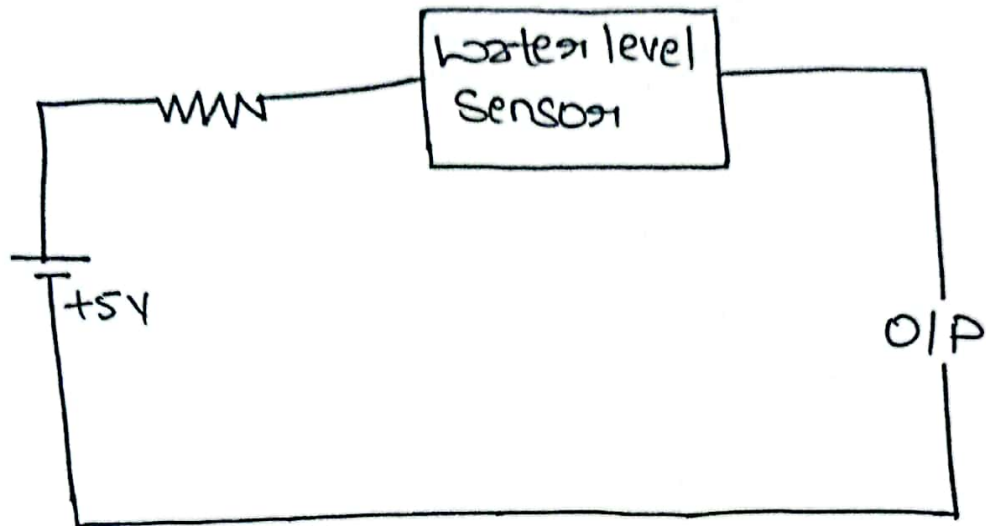

Observation:

Depth (in cm)	observed Voltage (V)	Strip Emerged in Water Initial/Dry
0	0	Half
0.5	2.8	
1.0	3.0	
1.5	3.3	
2.0	3.32	
2.5	3.4	full
3.0	3.5	

Result:- Water Level sensor completed successfully.

24/9/24

TITLE : Light Sensor

Expt No. : 3

Date : 03/28/2022

~~Procedure~~

Aim:-

- a. conduct an experiment to determine the sensitivity of the light sensor.
- b. Analyze the application of light sensor using LDR.


Components Required:

S.NO	Components Name	Quantity
i	LDR	1
ii	Voltmeter	1
iii	Buzzer	1
iv	connecting wires	2
v	Trainer Kit	1
vi	Multimeter	1

Marks :

Staff :

Circuit Diagram:-

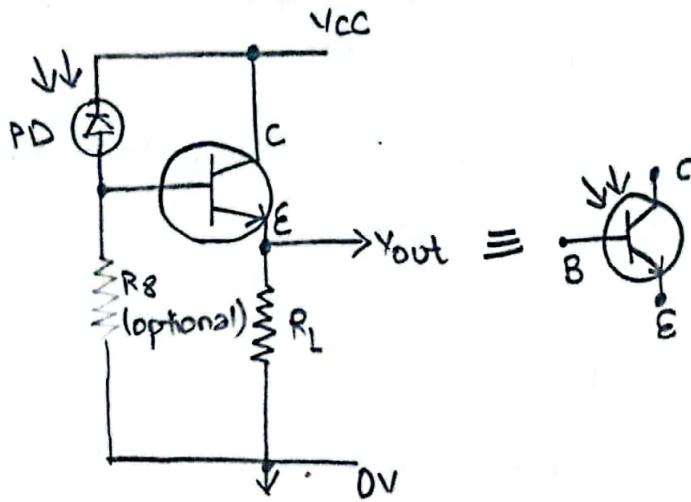

TITLE : Light Sensor.

Expt No. : 3

Date : 03/28/2022

S.No.	Intensity of the light	o/p voltage	Status of the Buzzer
1	Low	0.8	High sound
2	Medium	0.19	Medium sound
3	high	0.06	No sound

Result: We successfully conducted light sensor.

Marks :

Staff :

TITLE : Ultrasonic Sensor

Expt No. : 4

Date : 27/10/2022

Aim:-

- a) conduct an experiment to determine the sensitivity of the Ultrasonic Sensor.
- b) Analyze the application of Ultrasonic Sensor using distance meter circuit.

Components Required:-

S.No.	Components Name	Quantity
1	Arduino Board	1
2	Ultrasonic Sensor	1
3	connecting Wires	6
4	Buzzer	1
5	program	


Procedure:-

- i) collect the components necessary to complete the circuit.
- ii) There are 4 pins in Ultrasonic Sensor i.e Trig, Echo, Vcc and GND.
- iii) Connect trigger in pin no. 6 and Echo in pin no. 7 as well as Vcc in 5V and GND in GND of the arduino board.

Marks :

Staff :

Circuit Diagram

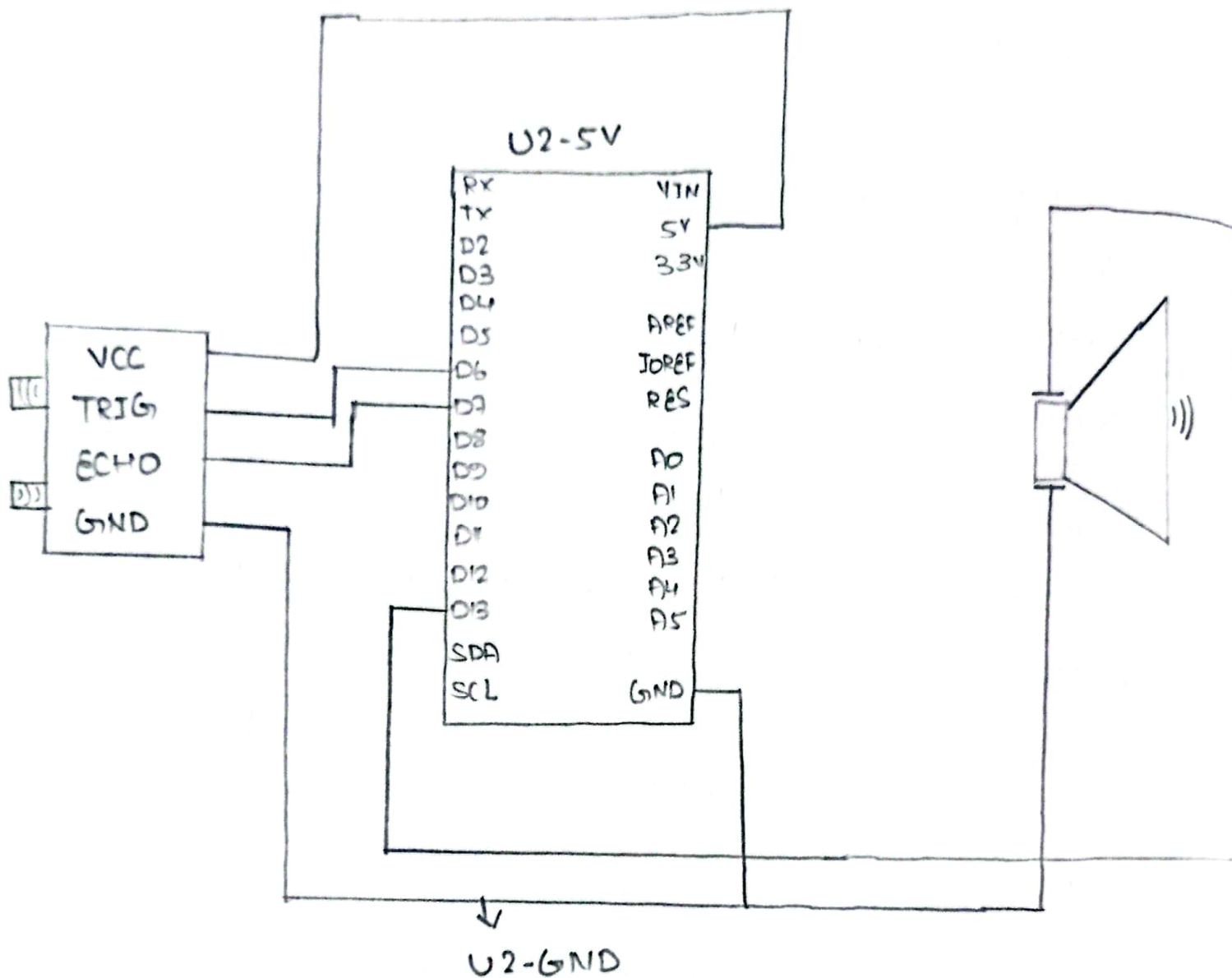

TITLE : Ultrasonic Sensor

Expt No 4

Date 27/10/2022

- iv) Connect the buzzer, one terminal in ground i.e cathode and anode in pin no.13 of Arduino Board.
- v) Simulate the program in Arduino Board.
- vi) Expose the sensor near and far from obstacles to take the measurements.
- vii) Repeats above steps by taking different measurements.

Program or Source Code:-

```
#define pingTrig 6
#define pingEcho 7
#define IdxValue 0
int led = 13;
void setup() {
  Serial.begin(9600);
  pinMode(pingTrig, OUTPUT);
  pinMode(pingEcho, INPUT);
  delay(200);
  pinMode(led, OUTPUT);
}
void loop() {
  long duration, inches, cm, value;
  digitalWrite(pingTrig, LOW);
```

Marks :

Staff :

Observation:

SI NO.	Centimeters	Inches	LED(ON/OFF)
1	3.8cm	1.5 inch	ON
2	42.7cm	16.4 inch	OFF
3	2.8cm	1.6 inch	ON
4	27.9cm	11.0 inch	ON
5	31.6cm	12.5 inch	OFF

TITLE UltraSonic Sensor

Expt No

4

Date

23/10/2022

```
delayMicroseconds(2);  
digitalWrite(pingTrig, HIGH);  
delayMicroseconds(10);  
digitalWrite(pingTrig, LOW);  
duration = pulseIn(pingEcho, HIGH);  
cm = duration / 29 / 2;  
inches = cm / 2.5;  
Serial.print("-->");  
Serial.print(cm);  
Serial.print("-->");  
Serial.print(inches);  
if (cm < 30) {  
    digitalWrite(led, HIGH);  
    delay(200);  
    digitalWrite(led, LOW);  
    delay(200);  
}
```

Result:- Sensitivity of the sensor was determined and output was verified.

Marks :

Staff :

TITLE : Temperature Sensor

Expt No. : 5

Date : 27/10/2022

Aim:

- a. Conduct an experiment to determine the sensitivity of the temperature sensor.
- b. Design a system to display the temperature in the location.

Components Required:

Sl. No	Components Name	Quantity
1	LM35 (Temperature sensor)	1
2	Connecting Wires	3
3	Arduino Board	1
4	Program	



Procedure:

- i) Collect the components necessary to complete the circuit.
- ii) Connect LM35 with Arduino Board.
- iii) There are 3 terminals in sensor i.e Vcc, Vout and GND.
- iv) Connect Vcc with 5V, GND with GND and Vout with A0 of Arduino Board.
- v) With the variation of temperature, Vout will change and simulate code.

Marks :

Staff :

Circuit diagram

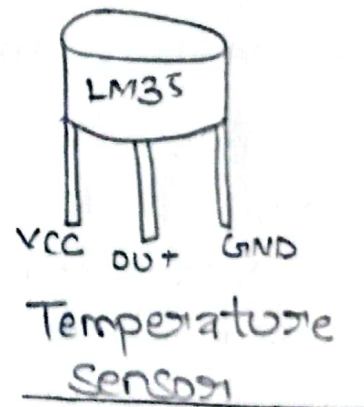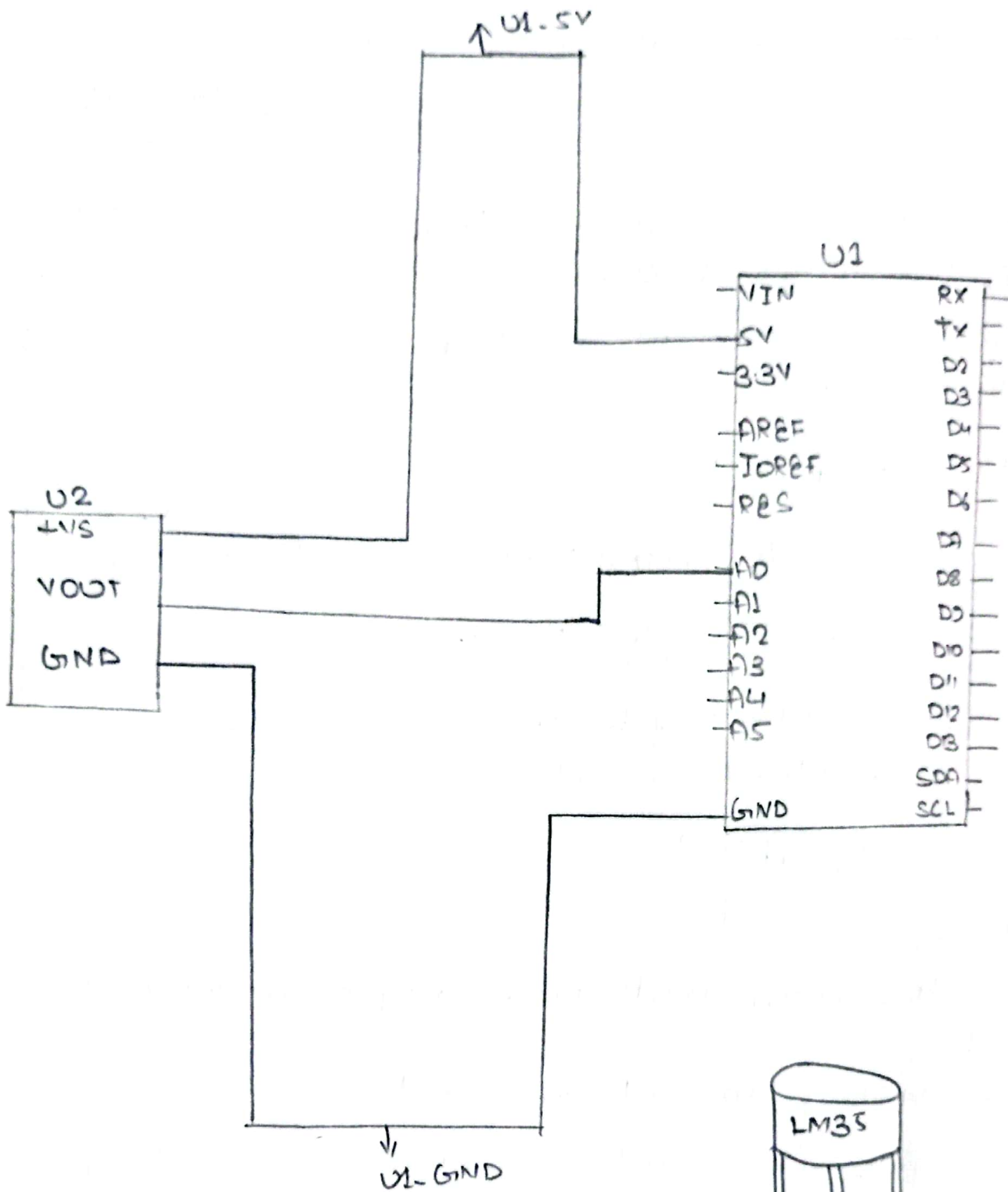

TITLE : Temperature Sensor

Expt No. : 5

Date : 22/10/2022

vi) Repeat above the steps by taking different Measurements.

program or Source Code:-

```
int val;  
int tempPin=1;  
void setup() {  
  Serial.begin(9600);  
}  
void loop() {  
  val = analogRead(tempPin);  
  float mv = (val / 1024.0) * 5000;  
  float cel = mv / 10;  
  float fahr = (cel * 9) / 5 + 32;  
  float kel = 273 + cel;  
  Serial.print("Temperature in Celsius =");  
  Serial.print(cel);  
  Serial.print(" * C");  
  Serial.println();  
  delay(1000);  
  Serial.print("Temperature in Fahrenheit =");  
  Serial.print(fahr);  
  Serial.print(" * F");  
  Serial.println();  
  Serial.print("Temperature in  
Kelvin =");
```

Marks :

Staff :

Observations:-

SI NO	Temp in cel(*c)	Fahrenheit (F)	Kelvin(K)
1	30°C	86°F	303.15K
2	23°C	73.4°F	296.15K
3	50°C	122°F	323.15K
4	96°C	204.8°F	369.15K

TITLE : Temperature Sensor

Expt No

5

Date

27/10/2022

```
Serial.print(Kel);  
Serial.print(" * K");  
Serial.println();  
delay(1000);
```

Result:- Sensitivity of the Temperature Sensor was determined and output in various scales were verified.

Marks :

Staff :